

Roll No. .... [ Total No. of Pages : 4

**EE-1846**

**B. Tech. (First Semester)**

**EXAMINATION, 2020**

**ELECTRICAL ENGINEERING**

*Time : Three Hours*

*Maximum Marks : 100*

**Note :** Attempt questions from both Sections as directed.

**Section—A**

**(Short Answer Type Questions)**

**Note :** Attempt any *ten* questions. Each question carries 4 marks.  $10 \times 4 = 40$

1. Explain Active and Passive elements.
2. Discuss different types of voltage and current sources.

**P. T. O.**


3. State and explain Kirchhoff's laws.
4. Define term : MMF, flux and reluctance.
5. Describe the analogies between electric and magnetic circuits.
6. State and explain Faraday's law of electromagnetic induction.
7. What is meant by leakage and fringing ?
8. Define the following :
  - (i) Q factor
  - (ii) Power factor
  - (iii) Active and Reactive Power
9. Draw the phasor diagrams for pure inductive and pure capacitive circuits.
10. What is a 3-phase system ? Give its necessity and advantages.
11. What is a function of Transformer ?
12. What do you understand by step-up and step-down transformer ?
13. State and explain super-position theorem.
14. State Thevenin's theorem.
15. State and prove maximum power transfer theorem.

## Section—B


## (Long Answer Type Questions)

**Note :** Attempt any *three* questions. Each question carries 20 marks.  $3 \times 20 = 60$

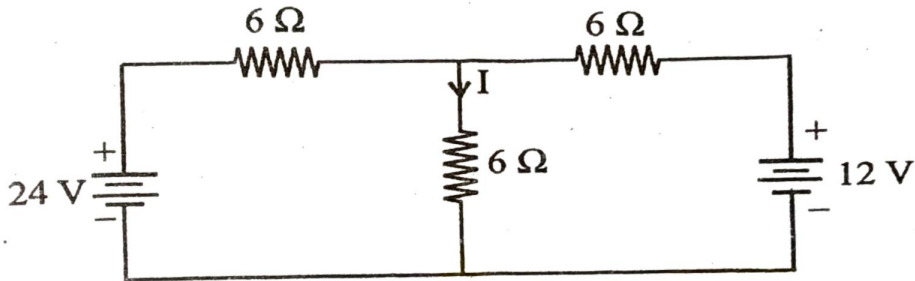1. Using superposition theorem find the current  $I$  in the given network :



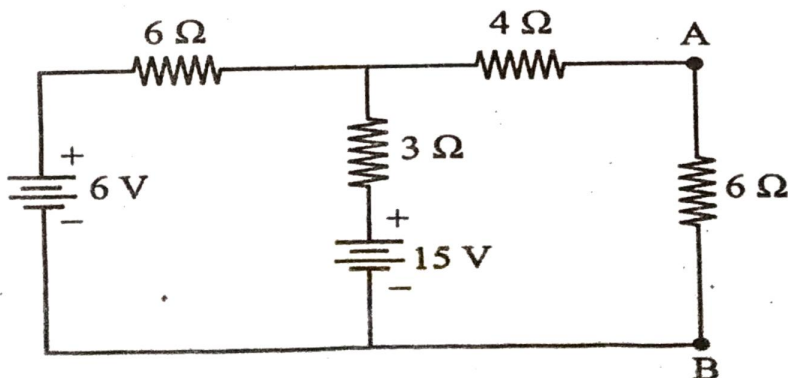2. Determine current through  $6\ \Omega$  resistance connected across AB terminals in the circuit shown, using Thevenin's theorem :



3. Explain the principle of operation and construction of a Transformer.
4. Explain the working of a Moving Iron Type Instrument.
5. Explain construction and working principle of DC motor.
6. Explain and derive the expression for (R-L-C) series circuit.