

A

EE-201

B.Tech. (Ist Year) (IInd Semester)

Examination – 2011

Electrical Engineering

Time: Three Hours

Maximum Marks: 100

n
x 100
S

Note: Attempt all Sections.

Section – A

Note: Attempt any ten questions. Each question carries four marks. (4x10=40)

1. Define:

- (a) Lumped and distributed circuits
- (b) Linear and non linear circuits


2. For ac input derive the expression of current and power factor for a series R-C circuit.

EE-201-S-430

3. (4) Derive the relation between line voltage and phase voltage in a star connected 3 ϕ balanced load supply.

4. Draw the equivalent circuit of a transformer referred to secondary side and define its circuit elements.

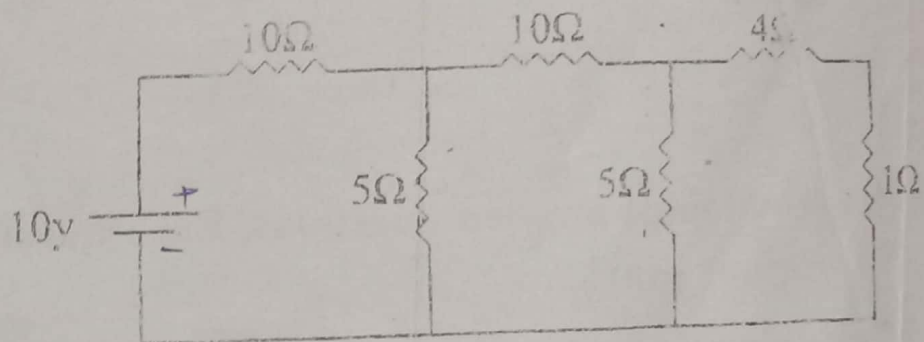5. Calculate the current through 1Ω resistance using loop method



6. Explain the working principle of a dc motor diagrammatically.


7. An inductor of resistance 10Ω and inductance of 0.6 H is in series with a capacitance $10\mu\text{F}$. If a voltage of 200 V is applied and the frequency is adjusted for resonance then find the current and voltage through capacitor.

8. If $V = 6 \cos(1000t - 30^\circ) V$ and

$i = 3 \cos(1000t + 10^\circ) A$, then

Identify the circuit element and find its value.

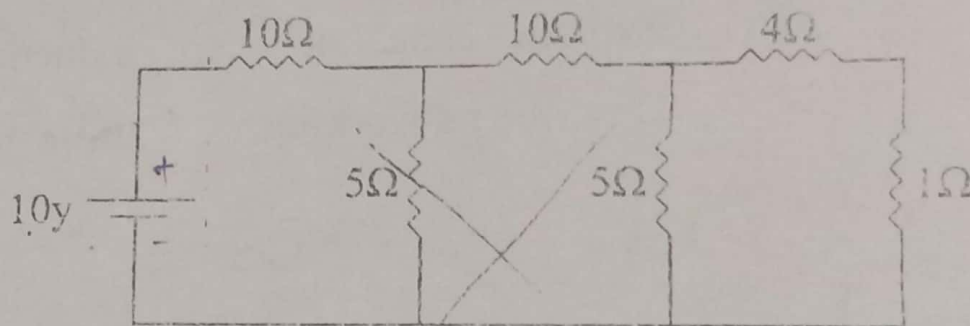9. Determine the mesh current I_1 & I_2 by mesh method.



10. A balanced star connected load of $(8+j6)\Omega$ per phase is connected to a balanced 3ϕ , 400V, 50Hz supply. Find:

(a) Line current (b) Power factor

11. Three identical resistors of 20Ω each are connected in star to a 415V, 50Hz 3ϕ supply. Calculate:

EE-201-S-430

$$\frac{\eta V_A \times \cos \phi}{\eta V_A \cos \phi + P_c + n^2 P_{cu}}$$

8

(ii) A 1000 VA transformer has a core loss of 15w and copper loss of 20w. Calculate its efficiency at 0.9 power factor lagging.

$$\frac{1000 \times 0.9}{1000 + 15 + 20}$$

(i) Explain the working of 3 ϕ induction motor and write the expression of slip.

$$s = \frac{n_s - n}{n_s}$$

(ii) Explain capacitor start induction motor.

Describe its working. (Start by line phase)

