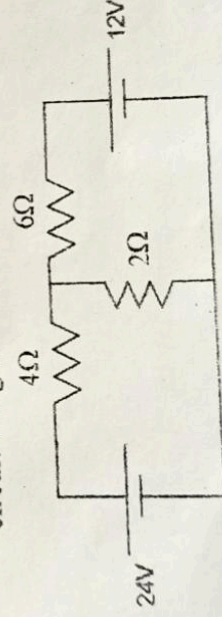


**EE-101/1846****B. Tech (Semester-I) Examination-2018  
Electrical Engineering***Time: Three Hours**Maximum Marks: 100***Note:** Attempt questions from all the sections.**Section-A****(Short Answer Type Questions)****Note:** Attempt any ten questions. Each question carries 4 marks. (4x10=40)

1. Explain active and passive element?


2. Explain the voltage division rule?

3. Determine the currents through various resistors of the circuit using mesh analysis.



EE-101/1846-D 40 P

4. State the Norton theorem.

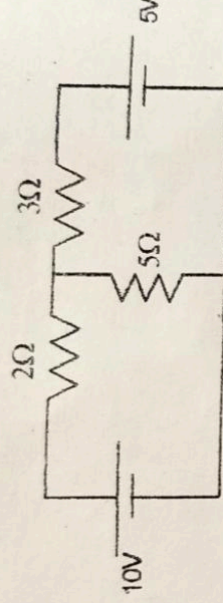

5. Using superposition theorem find the current through resistance  $5\pi$ .
6. Explain delta to star conversion?
7. What is reluctance and relative permeability?
8. Differentiate magnetic and electric circuit.
9. Explain B-H curve and saturation in brief.
10. Drive the R.M.S value of sinusoidal wave?



11. ✓ State active power and true power.
12. Find the Q-factor of resonant series circuit.
13. ✓ Drive the EME equation of transformer.
14. ✓ Drive the expression of maximum efficiency of transformer.
15. A six-pole lap wound D.C. generator has 720 conductors, a flux of 40 mWb/pole is driven at 400 r.p.m. find the generated E.M.F..

#### Section-B

##### (Long Answer Type Questions)

Note: Attempt any three questions. Each question carries 20 marks. (20x3=60)

- ✓ (a) Explain the moving Iron Instrument.
- ✓ (b) Explain the working of PMMC.

2. (a) Drive the equation of D.C. machine.  
(b) Drive Resonance in R-L-C Series circuit.
3. Explain the working principle of synchronous motor
4. Explain the speed torque characteristic of synchronous motor. Explain the V-Curve.
5. (a) Drive the expression of maximum power transfer theorem.  
(b) Write down the merits and demerits of moving iron Instrument.
6. Explain the following-
  - (i) Thevenin theorem
  - (ii) Series R-L-C Circuit
  - (iii) Eddy current Losses
  - (iv) Series motor